

# RAQ Issue 184: How a 16-Bit Output Module with Voltage and Current Outputs Can Be Controlled with Full Isolation from the Microcontroller

Thomas Brand, Field Applications Engineer

## Question:

How could I design a microcontroller-controlled isolated 16-bit output module?



## Answer:

Use the 3-chip solution for the [AD5422](#) DAC.

Whether in buildings or on production floors, programmable controllers are needed everywhere today to regulate various processes, machines, and systems. This involves programmable logic controllers (PLCs) or distributed control system (DCS) modules to which the devices are connected. To control these devices, the PLCs and DCS modules usually have output modules with current outputs, voltage outputs, or a combination of both. Industrial control modules cover the standard analog output voltage and current ranges of  $\pm 5$  V,  $\pm 10$  V, 0 V to 5 V, 0 V to 10 V, 4 mA to 20 mA, and 0 mA to 20 mA. Especially in the industrial sector, galvanic isolation of the microcontroller and the output peripherals is often required.

Classic solutions provide for a discrete design to convert the digital signals from the microcontroller to analog signals, or provide the different analog outputs, and to realize the galvanic isolation. However, compared with integrated solutions, a discrete design exhibits many disadvantages. For example, the large number of components results in high system complexity, a large board size, and high costs. Additional characteristics such as short-circuit capability or even fault diagnostics bring these drawbacks to the fore.

A better solution is to integrate as many functions as possible on a single chip, as is done, for example, with the AD5422, a high precision, 16-bit DAC from Analog Devices Inc. (ADI). In addition to the digital-to-analog conversion, it also offers a fully integrated programmable current source and a programmable voltage output, and thus meets the requirements of industrial process control applications.

Figure 1 shows an example circuit for fully isolated control of an analog output stage of an output module. It is especially suitable for PLCs and DCS modules in process control applications requiring standard current outputs of 4 mA to 20 mA and unipolar or bipolar output voltage ranges. The AD5422 is used here in combination with the [ADuM1401](#) quad-channel digital isolation module.

The outputs of the AD5422 16-bit DAC are configurable via a serial peripheral interface (SPI). The module also has integrated diagnostic functions, which can be useful in industrial environments. The required insulation resistance between the microcontroller and the DAC is achieved with the ADuM1401, whose four channels are used for the SPI connection to the AD5422: three channels (LATCH, SCLK, and SDIN) transmit the data and the fourth channel (SDO) receives the data.

Especially in industrial applications, robust outputs that are resistant to high interference voltages must be provided. The requirements for robustness are set forth in standards such as IEC 61000, which specifies, for example, the requirements with respect to electromagnetic compatibility (EMC). To comply with these standards, it is necessary to have additional external protective circuits at the outputs. One possibility for protective circuitry is shown in Figure 2.



VISIT [ANALOG.COM](http://ANALOG.COM)

