

# Low-Power, Unity-Gain Difference Amplifier Implements Low-Cost Current Source

By David Guo

In “Difference Amplifier Forms Heart of Precision Current Source,” published in *Analog Dialogue* in September 2009, the AD8276 unity-gain difference amplifier and AD8603 micropower op amp implement a precision current source. Figure 1 shows how the circuit can be simplified for use in low-cost, low-current applications.

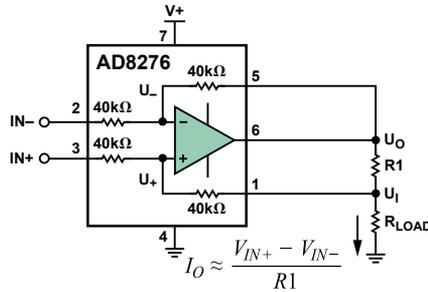


Figure 1. Simple current source for low-cost and low-current applications.

The output current,  $I_O$ , is approximately equal to the differential input voltage,  $V_{IN+} - V_{IN-}$ , divided by  $R1$ , as shown in the following derivation.

$$\frac{V_{IN-} - U_-}{40k} = \frac{U_- - U_O}{40k} \Rightarrow U_- = \frac{V_{IN-} + U_O}{2}$$

$$\frac{V_{IN+} - U_+}{40k} = \frac{U_+ - U_I}{40k} \Rightarrow U_+ = \frac{V_{IN+} + U_I}{2}$$

$$U_- = U_+ \Rightarrow V_{IN+} - V_{IN-} = U_O - U_I$$

Thus, the differential input voltage appears across  $R1$ .

$$R1 \ll 40k \Rightarrow I_O \approx I_{R1} \Rightarrow I_O \approx \frac{V_{IN+} - V_{IN-}}{R1}$$

## Experimental Setup

- AD5750EVB (AD5750 driver and AD5662 16-bit nanoDAC<sup>®</sup>) provides a bipolar input to the AD8276.
- OI-857 multimeter measures input voltage, output voltage, and resistance.
- The nominal values of  $R1$  and  $R_{LOAD}$  are 280  $\Omega$  and 1 k $\Omega$ , respectively; the measured values are 280.65  $\Omega$  and 997.11  $\Omega$ , respectively.
- The output current is calculated by dividing the measured voltage by  $R_{LOAD}$ .

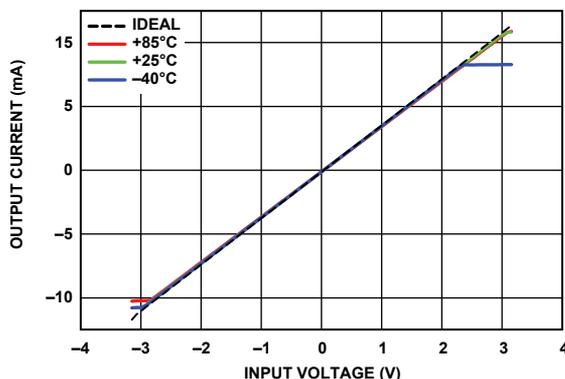


Figure 2. Ideal and real output current vs. differential input voltage.

## Experimental Results

Figure 2 shows the output current vs. the input voltage. The differential input voltage, which varies from  $-3.2$  V to  $+3.2$  V, is plotted on the X-axis; the output current is plotted on the Y-axis. The four lines show the ideal current and the real outputs at  $-40^\circ\text{C}$ ,  $+25^\circ\text{C}$ , and  $+85^\circ\text{C}$ .

Figure 3 shows the output current error vs. the input voltage. The three lines show the error at  $-40^\circ\text{C}$ ,  $+25^\circ\text{C}$ , and  $+85^\circ\text{C}$ .

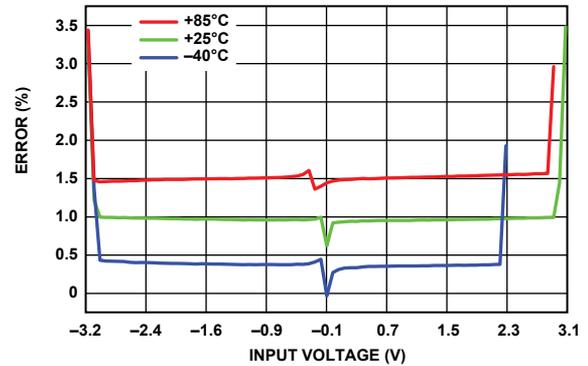


Figure 3. Output current error vs. input voltage.

The real output current is limited by the short-circuit output current of the AD8276, as shown in Figure 4. Here, the short-circuit current is about 8 mA at  $-40^\circ\text{C}$ .

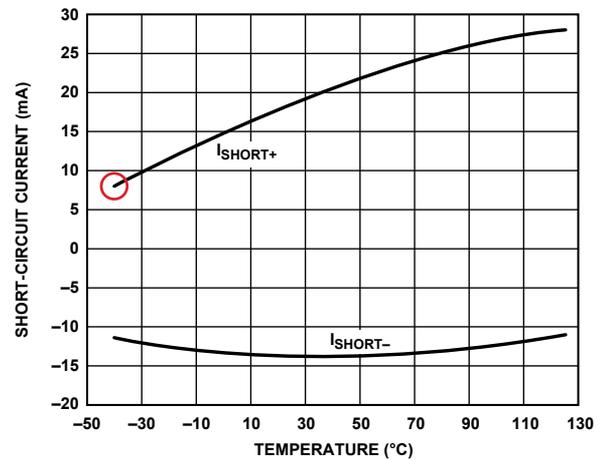


Figure 4. AD8276 short-circuit output current vs. temperature.

## Conclusion

By removing the external boost transistor and buffer and adding a single resistor, one can use the AD8276 to construct a low-cost, low-current source with a total error less than about 1.5% over the  $-40^\circ\text{C}$  to  $+85^\circ\text{C}$  temperature range. The output current range over temperature is about  $-11$  mA to  $+8$  mA when powered with a  $\pm 15$ -V supply. A unipolar source could be created with a single  $+5$  V supply.

## Author

**David Guo** [[david.guo@analog.com](mailto:david.guo@analog.com)] is a field applications engineer in ADI’s China Applications Support Team in Beijing. After earning a master’s degree in electronic and mechanism engineering from Beijing Institute of Technology, David spent two years as a navigation terminal hardware engineer at Changfeng Group. He joined ADI in 2007.

