

**High Performance, 12-Bit, 500 MSPS Wideband Receiver with Antialiasing Filter**

**CIRCUIT FUNCTION AND BENEFITS**

The circuit shown in Figure 1 is a wideband receiver front end based on the ADA4960-1 ultralow noise differential amplifier driver and the AD9434 12-bit, 500 MSPS analog-to-digital converter (ADC). The third-order Butterworth antialiasing filter is optimized based on the performance and interface requirements of the ampli-

fier and ADC. The total insertion loss due to the filter network, transformer, and other resistive components is only 1.2 dB.

The overall circuit has a bandwidth of 290 MHz with a pass-band flatness of 1 dB. The SNR and SFDR measured with a 140 MHz analog input are 64.1 dBFS and 70.4 dBc, respectively.

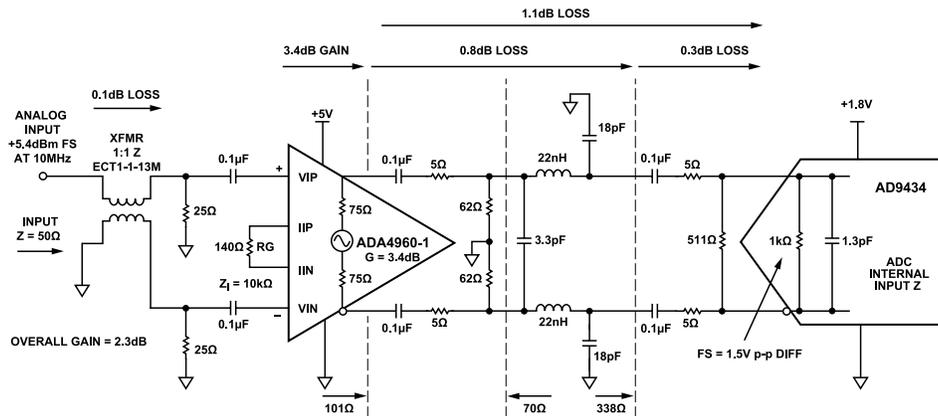


Figure 1. 12-Bit, 500 MSPS Wideband Receiver Front End (Simplified Schematic: All Connections and Decoupling Not Shown) Gains, Losses, and Signal Levels Measured Values at 10 MHz

**TABLE OF CONTENTS**

Circuit Function and Benefits.....	1	Passive Component and PC Board Parasitic	
Circuit Description.....	3	Considerations.....	5
Filter and Interface Design Procedure.....	4		
Circuit Optimization Techniques and Trade-			
Offs.....	5		

**REVISION HISTORY****5/2024—Rev. A to Rev. B**

Converted Document from CN-0238 to AN-2534 (Universal).....	1
Deleted Evaluation and Design Support Section.....	1
Deleted Common Variations Section, Circuit Evaluation and Test Section, Learn More Section, and Data Sheets and Evaluation Boards Section.....	5

**CIRCUIT DESCRIPTION**

The circuit accepts a single-ended input and converts it to differential using a wide bandwidth (3 GHz) M/A-COM ECT1-1-13M 1:1 transformer. The 5 GHz ADA4960-1 differential amplifier has a differential input impedance of 10 kΩ. Gain can be adjusted from 0 dB to 18 dB with the selection of the external gain-setting resistor, RG. The output impedance is 150 Ω differential.

The ADA4960-1 is an ideal driver for the AD9434, and the fully differential architecture through the low-pass filter and into the ADC provides good high frequency common-mode rejection, as well as minimizes second-order distortion products. The ADA4960-1 provides a gain of 0 dB to 18 dB, depending on the external gain resistor. In the circuit, a gain of 3.4 dB was used to compensate for the insertion loss of the filter network (1.1 dB) and the transformer (0.1 dB), providing an overall signal gain of 2.3 dB. An input signal of approximately 5.4 dBm produces a full-scale 1.5 V p-p differential signal at the ADC input.

The antialiasing filter is a third-order Butterworth filter designed with a standard filter design program. A Butterworth filter was chosen because of its flat response within the pass band. A third order filter yields an ac noise bandwidth ratio of 1.05 and can be designed with the aid of several free filter programs such as Nuhertz Technologies Filter Free or the Quite Universal Circuit Simulator (Qucs) Free Simulation.

In order to achieve best performance, the ADA4960-1 should be loaded with a net differential load of 100 Ω. The 5 Ω series resistors isolate the filter capacitance from the amplifier output, and the 62 Ω resistors in parallel with the downstream impedance yield a net load impedance of 101 Ω when added to the 10 Ω series resistance.

The 5 Ω resistors in series with the ADC inputs isolate internal switching transients from the filter and the amplifier. The 511 Ω resistor in parallel with the ADC serves to reduce the input impedance of the ADC for more predictable performance.

The third-order Butterworth filter was designed with a source impedance of 70 Ω, a load impedance of 338 Ω, and a 3 dB bandwidth of 360 MHz. The calculated values from the program are shown in Figure 2.

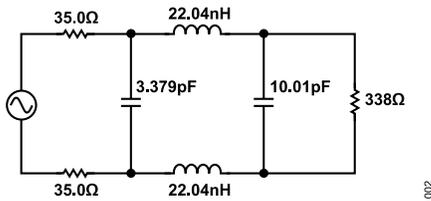


Figure 2. Design for Third-Order Differential Butterworth Filter with  $Z_s = 70 \Omega$ ,  $Z_L = 338 \Omega$ ,  $F_C = 360 \text{ MHz}$

The values chosen for the filter’s passive components were the closest standard values to those generated by the program.

The internal 1.3 pF capacitance of the ADC was subtracted from the value of the second shunt capacitor (10.01 pF) to yield a value of 8.71 pF. In the circuit, this capacitor was realized using two 18 pF

capacitors connected to ground as shown in Figure 1. This provides the same filtering effect, as well as offering some ac common-mode rejection.

The measured performance of the system is summarized in Table 1, where the 3 dB bandwidth is 290 MHz. The total insertion loss of the network is approximately 1.1 dB. The bandwidth response is shown in Figure 3; the SNR and SFDR performance are shown in Figure 4.

Table 1. Measured Performance of the Circuit

Performance Specs at 1.5 V p-p FS	Final Results
Cutoff Frequency (-3 dB)	290 MHz
Pass-Band Flatness (6 MHz to 200 MHz)	1 dB
SNRFS at 140 MHz	64.1 dBFS
SFDR at 140 MHz	70.4 dBc
H2/H3 at 140 MHz	85.0 dBc/70.4 dBc
Overall Gain at 10 MHz	2.3 dB
Input Drive at 10 MHz	5.4 dBm

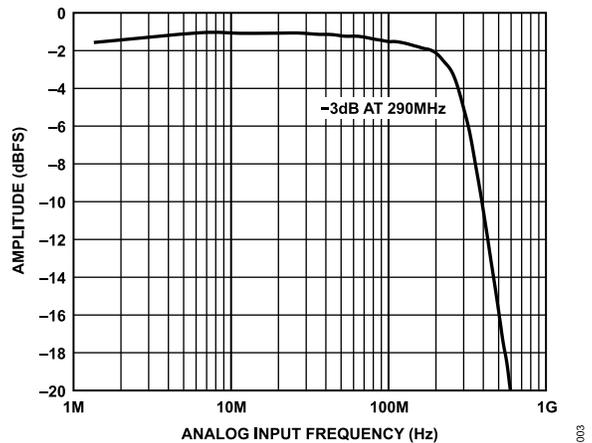


Figure 3. Pass-Band Flatness Performance vs. Frequency

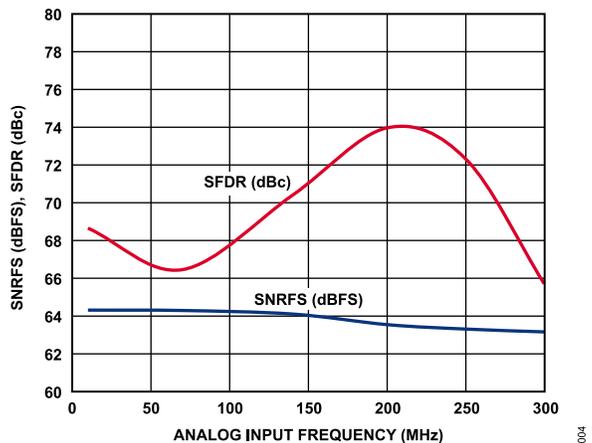


Figure 4. SNR/SFDR Performance vs. Frequency

**FILTER AND INTERFACE DESIGN PROCEDURE**

To achieve optimum performance (bandwidth, SNR, and SFDR), there are certain design constraints placed on the general circuit by the amplifier and the ADC:

1. The amplifier should see the correct dc load recommended by the data sheet for optimum performance.
2. The correct amount of series resistance must be used between the amplifier and the load presented by the filter. This is to prevent undesired peaking in the pass band.
3. The input to the ADC should be reduced by an external parallel resistor, and the correct series resistance should be used to isolate the ADC from the filter. This series resistor also reduces peaking.

The generalized circuit shown in Figure 5 applies to most high speed differential amplifier/ADC interfaces and will be used as a basis for the discussion. This design approach tends to minimize the insertion loss of the filter by taking advantage of the relatively high input impedance of most high speed ADCs and the relatively low impedance of the driving source (amplifier).

The basic design process is as follows:

1. Select the external ADC termination resistor  $R_{TADC}$  so that the parallel combination of  $R_{TADC}$  and  $R_{ADC}$  is between 200  $\Omega$  and 400  $\Omega$ .
2. Select  $R_{KB}$  based on experience and/or the ADC data sheet recommendations, typically between 5  $\Omega$  and 36  $\Omega$ .
3. Calculate the filter load impedance using:

$$Z_{AAFL} = R_{TADC} \parallel (R_{ADC} + 2R_{KB})$$

4. Select the amplifier external series resistor  $R_A$ . Make  $R_A$  less than 10  $\Omega$  if the amplifier differential output impedance is 100

$\Omega$  to 200  $\Omega$ . Make  $R_A$  between 5  $\Omega$  and 36  $\Omega$  if the output impedance of the amplifier is 12  $\Omega$  or less.

5. Select  $R_{TAMP}$  so that the total load seen by the amplifier,  $Z_{AL}$ , is optimum for the particular differential amplifier chosen using the equation:

$$Z_{AL} = 2R_A + (Z_{AAFL} \parallel 2R_{TAMP})$$

6. Calculate the filter source resistance:

$$Z_{AAFS} = 2R_{TAMP} \parallel (Z_O + 2R_A)$$

7. Using a filter design program or tables, design the filter using the source and load impedances,  $Z_{AAFS}$  and  $Z_{AAFL}$ , type of filter, bandwidth, and order. Use a bandwidth that is about 40% higher than one-half the sampling rate to ensure flatness in the frequency span between dc and  $f_s/2$ .
8. The internal ADC capacitance,  $C_{ADC}$ , should be subtracted from the final shunt capacitor value generated by the program. The program will give the value  $C_{SHUNT2}$  for the differential shunt capacitor. The final common-mode shunt capacitance is

$$C_{AAF2} = 2(C_{SHUNT2} - C_{ADC})$$

After running these preliminary calculations, the circuit should be given a quick review for the following items.

1. The value of  $C_{AAF2}$  should be at least 10 pF so that it is several times larger than  $C_{ADC}$ . This minimizes the sensitivity of the filter to variations in  $C_{ADC}$ .
2. The ratio of  $Z_{AAFL}$  to  $Z_{AAFS}$  should not be more than about 7 so that the filter is within the limits of most filter tables and design programs.
3. The value of  $C_{AAF1}$  should be at least 5 pF to minimize sensitivity to parasitic capacitance and component variations.
4. The inductor,  $L_{AAF}$ , should be a reasonable value of at least several nH.

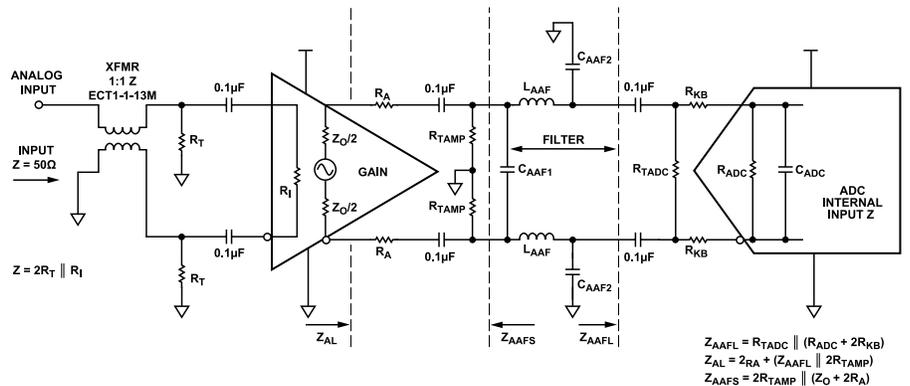


Figure 5. Generalized Differential Amplifier/ADC Interface with Low-Pass Filter

In some cases, the filter design program may provide more than one unique solution, especially with higher order filters. The solution that uses the most reasonable set of component values should always be chosen. Also, choose a configuration that ends in a shunt capacitor so that it can be combined with the ADC input capacitance.

## CIRCUIT OPTIMIZATION TECHNIQUES AND TRADE-OFFS

The parameters in this interface circuit are very interactive; therefore, it is almost impossible to optimize the circuit for all key specifications (bandwidth, bandwidth flatness, SNR, SFDR, and gain). However, the peaking, which often occurs in the bandwidth response, can be minimized by varying  $R_A$  and  $R_{KB}$ .

The pass-band peaking is reduced as the value of the output series resistance,  $R_A$ , is increased. However, as the value of this resistance increases, there is more signal attenuation, and the amplifier must drive a larger signal to fill the ADC's full-scale input range.

The value of  $R_A$  also affects SNR performance. Larger values, while reducing the bandwidth peaking, tend to slightly increase the SNR because of the higher signal level required to drive the ADC full scale.

Select the  $R_{KB}$  series resistor on the ADC inputs to minimize distortion caused by any residual charge injection from the internal sampling capacitor within the ADC. Increasing this resistor also tends to reduce bandwidth peaking.

However, increasing  $R_{KB}$  increases signal attenuation, and the amplifier must drive a larger signal to fill the ADC input range.

Another method for optimizing the pass-band flatness is to vary the filter shunt capacitor,  $C_{AAF2}$ , by a small amount.

Normally, the ADC input termination resistor,  $R_{TADC}$ , is selected to make the net ADC input impedance between 200  $\Omega$  and 400  $\Omega$ . Making it lower reduces the effect of the ADC input capacitance and may stabilize the filter design; however, it increases the insertion loss of the circuit. Increasing the value also reduces peaking.

Balancing these trade-offs can be somewhat difficult. In this design, each parameter was given equal weight; therefore, the values chosen are representative of the interface performance for all the design characteristics. In some designs, different values may be chosen to optimize SFDR, SNR, or input drive level, depending on system requirements.

Note that the signal in this design is ac coupled with the 0.1  $\mu\text{F}$  capacitors to block the common-mode voltages between the amplifier, its termination resistors, and the ADC inputs. Refer to the [AD9434](#) data sheet for further details regarding common-mode voltages.

## PASSIVE COMPONENT AND PC BOARD PARASITIC CONSIDERATIONS

The performance of this or any high speed circuit is highly dependent on proper PCB layout. This includes, but is not limited to, power supply bypassing, controlled impedance lines (where required), component placement, signal routing, and power and ground planes. See [Tutorial MT-031](#) and [Tutorial MT-101](#) for more detailed information regarding PCB layout for high speed ADCs and amplifiers.

Low parasitic surface-mount capacitors, inductors, and resistors should be used for the passive components in the filter. The inductors chosen are from the Coilcraft 0603CS series. The surface-mount capacitors used in the filter are 5%, C0G, 0402-type for stability and accuracy.