

# DESIGN NOTES

## Inexpensive Circuit Charges Lithium-Ion Cells – Design Note 188

David Bell

### Introduction

A single Lithium-Ion cell is often the battery of choice for portable equipment because of its high energy density. The 3V to 4.1V provided by a Lithium-Ion cell is also a good match for modern low voltage circuits, often simplifying the power supply. Despite these advantages, designers are often frustrated when attempting to design precision charging circuitry that meets battery manufacturers' specifications. Figure 2 is a simple, cost-effective linear charger that satisfies these precision Lithium-Ion charging requirements.

Lithium-Ion cell manufacturers generally recommend a constant-current/constant-voltage (CC/CV) charging technique. Although conceptually simple, charging a Lithium-Ion cell requires very accurate control of the float voltage to obtain high capacity with long cycle life. If the voltage is too low, the cell will not be fully charged; if the voltage is too high, the cycle life is significantly degraded. Excessive voltage to the cell can also result in venting and other hazardous conditions (specific hazards depend upon the cell's construction and chemistry).

Figure 1 depicts CC/CV charging characteristics for a typical Lithium-Ion cell. A fully discharged cell will initially be charged by a constant current, since the cell's voltage is below the 4.1V constant-voltage limit. (Most Lithium-Ion cells require either a 4.1V or 4.2V float voltage, depending on the cell's chemistry.) Once the cell's voltage rises to the float voltage of 4.1V, the charger limits further rise in terminal voltage and the charging current naturally begins to fall off. Most battery

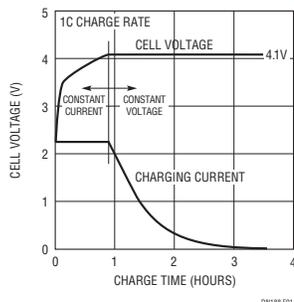


Figure 1. Typical Lithium-Ion Charge Characteristics

manufacturers recommend that charging be terminated roughly one hour after the current has fallen to 10% of its peak value. Alternatively, a timer can be started when charging begins, with time-out used to suspend charging once sufficient time has elapsed to charge a fully depleted cell.

### Circuit Description

Figure 2 depicts a simple and inexpensive linear charger that can be used to charge a single Lithium-Ion cell. The circuit provides constant-current/constant-voltage (CC/CV) charging from an inexpensive, unregulated 6V wall adapter. The charger is built around a single LTC<sup>®</sup>1541, which contains a voltage reference, op amp and comparator. The high accuracy voltage reference ( $\pm 0.4\%$ ) regulates the battery float voltage to  $\pm 1.2\%$ , as required by most Lithium-Ion battery manufacturers. Even tighter accuracy can be obtained by specifying higher accuracy for feedback divider resistors R6 and R7. The charger may be configured to float at either 4.1V or 4.2V by changing the value of R6. Use 252k for a 4.1V float voltage; use 261k for a 4.2V float voltage.

Transistor Q1 is used to regulate battery charging current. Q1's base current is controlled by the op amp output (Pin 1) and buffered by transistor Q2 for additional current gain. Diode D1 is needed to prevent reverse current flow when the wall adapter is unplugged or unpowered. Because this is a linear regulator, the designer must consider power dissipation in Q1. As shown with a 6V wall adapter, Q1 dissipates a maximum of about 1W and can be heat sunk directly to the printed circuit board. Higher current levels or higher input voltages will increase dissipation and additional heat sinking will be needed.

Battery charging current is sensed by R11 and fed to the op amp's noninverting input via R10. IC1's internal 1.2V reference voltage is divided to 44mV by R4 and R2 and connects to the op amp's inverting input. The op amp compares the current sense voltage against the 44mV

LT, LT, LTC, LTM, Linear Technology and the Linear logo are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.

