

DESIGN NOTES

Sense Milliamps to Kiloamps and Digitize to 12 Bits – Design Note 227

Richard Markell and Glen Brisebois

Introduction

The LT[®]1787 high side current sense amplifier provides a precision measurement of current into or out of a power source. The part generates an output voltage that is directly proportional to the current flowing through an external current sense resistor. With a miniscule 40 μ V (typical) input offset voltage, the LT1787 has a better than 12-bit, zero-cross accurate dynamic range at 250mV full-scale input. A hefty 60V maximum supply voltage specification allows the part to be used not only in low voltage battery applications but also in higher voltage telecom and industrial applications. Independent V_{EE} and V_{BIAS} pins make the application of the LT1787 extremely versatile.

The device is self-powered from the supply that it is monitoring and requires only 60 μ A of supply current. The power supply rejection ratio of the LT1787 is in excess of 120dB. The part has a fixed voltage gain of 8 from input to output.

Additional LT1787 features include provisions for input noise filtering (both differential and common mode) and the ability to operate over a very wide supply range of 2.5V to 60V. A functional diagram of the part and its theory of operation is detailed in the side bar. The part is available in both 8-lead SO and MSOP packages.

Operation with an A/D Converter

Figure 1 shows a detailed schematic of a high resolution (12-bit), bidirectional current-to-bits converter using an LT1787, the LT1783 SOT-23 1.2MHz micropower, rail-to-rail op amp and the LTC1404 SO-8 packaged, 12-bit analog-to-digital converter with shutdown. The circuit, as shown, allows digitization of input current from approximately $-3A$ to approximately $2A$ with 12-bit resolution.

The LT1787's output voltage is buffered by the LT1783, filtered and applied to the LTC1404's A_{IN} pin. The precision bias voltage applied to the V_{BIAS} pin of the LT1787 is obtained from the LTC1404's reference output and is typically 2.43V. This bias voltage sets the zero-current output of the LT1787 to 2.43V, or approximately mid-range for the A-to-D converter, allowing measurement of current in both the positive and negative directions. Note that the LTC1404's internal reference voltage is 4.096V; thus the output of the converter is 1 count per millivolt of input voltage from the LT1787's output, or 8 counts/mV of input voltage across R_{SENSE} . Zero sense-current translates to 2.43V or 2430 counts from the converter. Full-scale positive current is 4096 counts and full-scale negative current is 0 counts.

LT, LT, LTC, LTM, Linear Technology and the Linear logo are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.

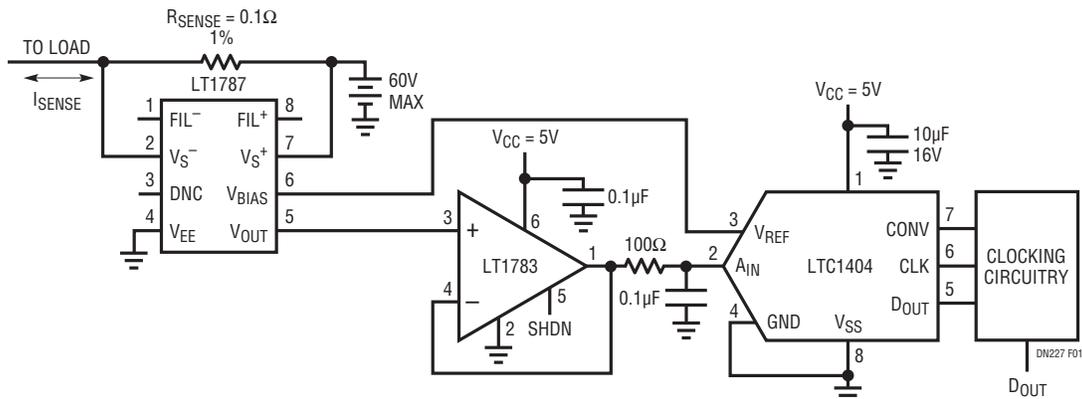


Figure 1. LT1787 Connected to LTC1404 ADC: Bidirectional Current-to-Bits Converter

Figure 2 shows current versus output code for the complete system. The LTC1404 has a digital interface consisting of the CLK and CONV input and the D_{OUT} serial digital output. The signals provide wide flexibility in allowing the part to be interfaced to most microprocessors and DSPs.

The output voltage, V_{OUT}, of the LT1787 is related to the input sense voltage by the following relationships:

$$V_{SENSE} = I_{SENSE} \cdot R_{SENSE}$$

$$V_{OUT} = 8(V_{SENSE}) + V_{BIAS}$$

Although a -3A to 2A range was selected for this illustration, other current ranges can be accommodated by a simple change in value of the sense resistor. The correct R_{SENSE} value is derived so that the product of the maximum sense current and the sense resistor value is equal to the desired maximum sense voltage (250mV for 12-bit resolution). For instance, the value of the sense resistor to sense a maximum current of 10A is 250mV/10A = 0.025Ω. The smallest measurable current is then 10A/4096 counts = 2.44mA/count. If only 10-bit resolution is desired, then the full-scale voltage can be reduced to 60mV and R_{SENSE} reduced to 0.006Ω. Ensure that the power dissipated in the sense resistor, I_{MAX}² • R_{SENSE}, does not exceed the maximum power rating of the resistor.

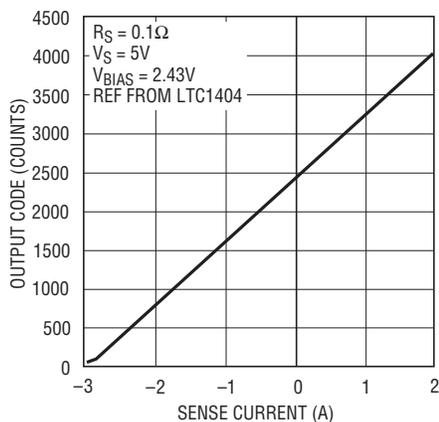


Figure 2. Current vs Output Code

Conclusion

The LT1787 high side current sense amplifier provides an easy-to-use method of sensing current with 12-bit resolution for a multiplicity of application areas. The part

can operate to 60V, making it ideal for higher voltage systems in telecom or industrial applications. Additionally, the part can find application in battery-powered, handheld equipment and computers, where the need for gauging the amount of current consumed and/or the amount of charge remaining in the battery is critical.

Theory of Operation (See Figure 3)

Inputs V_S⁺ and V_S⁻ apply the sense voltage to matched resistors R_{G1} and R_{G2}. The opposite ends of resistors R_{G1} and R_{G2} are forced to be at equal potentials by the voltage gain of amplifier A1. The currents through R_{G1} and R_{G2} are forced to flow through transistors Q1 and Q2 and are summed at node V_{OUT} by the 1:1 current mirror. The net current from R_{G1} and R_{G2} flowing through resistor R_{OUT} gives a voltage gain of eight. Positive sense voltages result in V_{OUT} being positive with respect to pin V_{BIAS}.

Pins V_{EE}, V_{BIAS} and V_{OUT} may be connected in a variety of ways to interface with subsequent circuitry. Split supply and single supply output configurations are easily supported.

Supply current for amplifier A1 is drawn from the V_S⁻ pin. The user may choose to include this current in the monitored current (through R_{SENSE}) by careful choice of connection polarity.

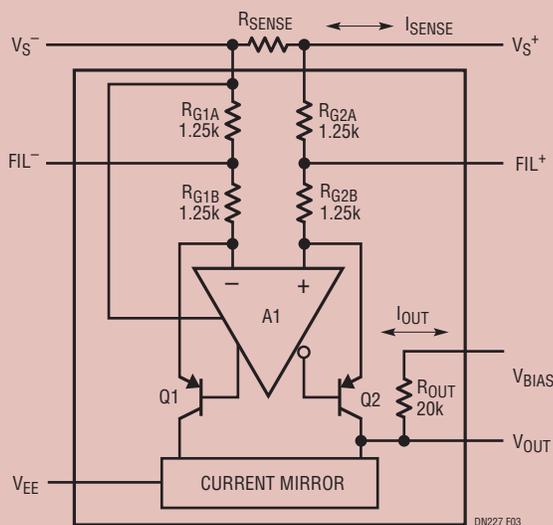


Figure 3. LT1787 Functional Diagram

Data Sheet Download

www.linear.com

For applications help,
call (408) 432-1900