

Keywords: charge pump, voltage doubler, tripler, low current applications, op amp, LCD circuit

## APPLICATION NOTE 297

# Tripler Converts 5V to 15V

Aug 17, 2000

*Abstract: This application note shows how to configure the MAX1683 to triple the input voltage for low-current applications while minimizing voltage drop.*

A similar version of this article appeared in the August 17, 2000 issue of *ECN* magazine.

By configuring a charge-pump voltage doubler as a tripler, you can readily derive 15V from 5V. A 15V rail is useful for powering op amps, LCD-bias circuits, and other low-current applications.

The connections in **Figure 1** configure the MAX1683 voltage doubler as a tripler. The no-load output voltage of the circuit is approximately  $3V_{IN} - 2V_D$ , where  $V_D$  is the voltage drop across one diode. Use Schottky diodes as shown to minimize  $V_D$  and its effect on output voltage.

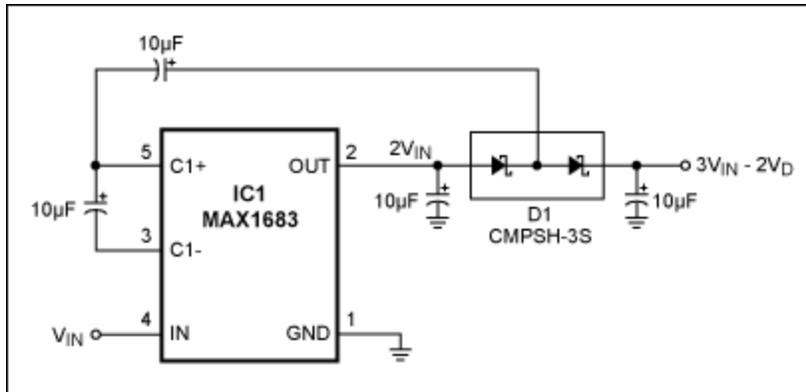


Figure 1. This circuit (almost) triples the input voltage for low-current applications.

Because the circuit's finite output impedance causes the output voltage to drop with load current (**Figure 2**), a practical limit for load current is approximately 30mA.

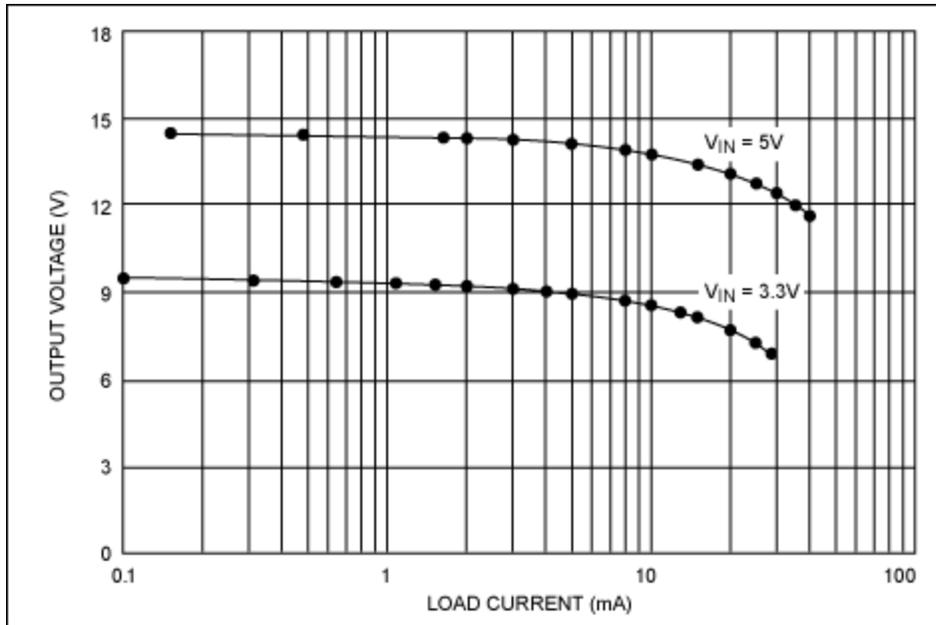


Figure 2. Finite output impedance causes a decline in voltage with increasing load current.

#### Related Parts

[MAX1683](#)

Switched-Capacitor Voltage Doublers

[Free Samples](#)

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 297: <http://www.maximintegrated.com/an297>

APPLICATION NOTE 297, AN297, AN 297, APP297, Appnote297, Appnote 297

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>