



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [A/D and D/A Conversion/Sampling Circuits](#) > APP 2013  
[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Voltage References](#) > APP 2013

Keywords: analog-to-digital converter, ADC, ADC accuracy, voltage reference scaling technique, ADC effective resolution, voltage divider, voltage reference

APPLICATION NOTE 2013

# Voltage Reference Scaling Technique Increases ADC Accuracy to Keep Costs Down

By: Franco Contadini  
Jun 20, 2013

*Abstract: In this design note a circuit uses a 10-bit ADC, voltage divider, and external reference to improve the ADC's virtual accuracy to 13 bits. The article shows a voltage scaling technique that extends 10-bit ADC range to 13 bits. The [MAX159](#) 10-bit ADC, [MAX5420](#) voltage divider, and [MAX6141](#) voltage reference are featured.*

A data acquisition board, in order to provide flexibility, must be able to accommodate various input voltage ranges. Handling low amplitude signals generally requires an increase in the number of bits of resolution, increasing cost.

This application note describes a simple circuit that uses a low cost 10-bit ADC but increases the virtual accuracy to 13-bit.

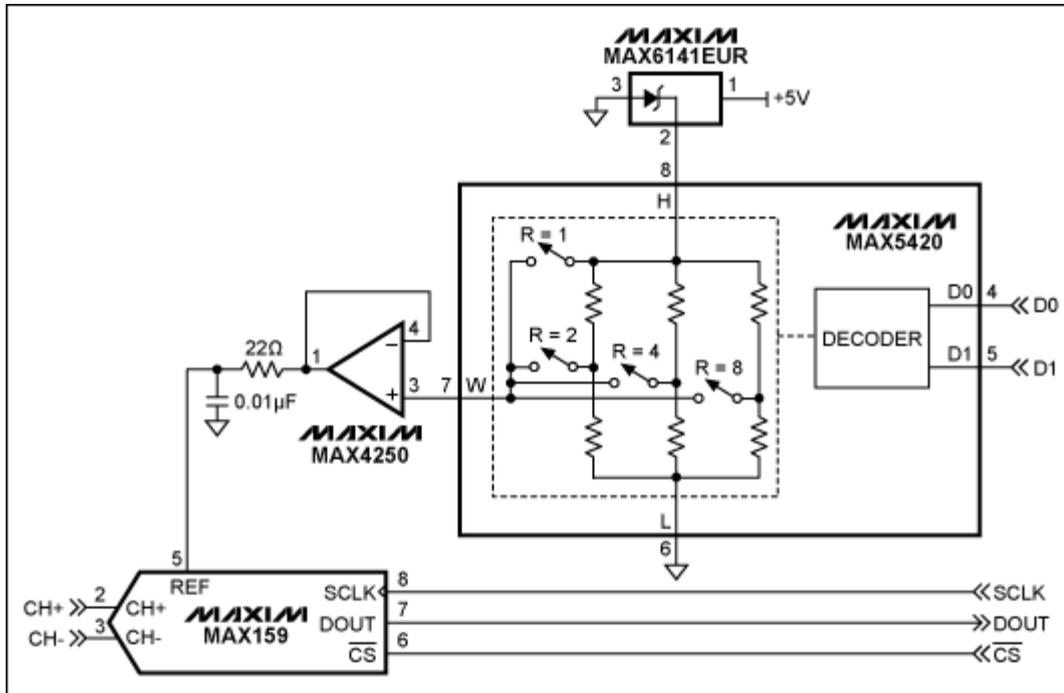


Figure 1.

1 LSB (least significant bit) for an ADC is  $FSR/2^n$ , where  $n$  is the number of bit. FSR (full-scale range) depends from the amplitude of the voltage reference. The input voltage range of the external reference for MAX159, a low power, 108ksps serial ADC available in  $\mu$ MAX<sup>®</sup>-8 package, is 0 to  $V_{DD} + 50mV$ . This large input range permits to accommodate different input range using a scaling technique.

The output of a low-cost 3-pin voltage reference is scaled using a digitally programmable voltage divider (MAX5420). This device provides four precision divider ratios of 1, 2, 4, 8. The ratio accuracy span from 0.025% to 0.5% according to the grade (A, B, C). The ratio is selected using the digital inputs D1, D0 as follows:

Table 1.

DIGITAL INPUTS		DIVIDER RATIO
D1	D0	
0	0	1
0	1	2
1	0	4
1	1	8

The reference voltage MAX6141 provides an output voltage of 4.096V. The size of 1 LSB using a divider ratio of 1 will be  $4.096/1024 = 4mV$ . This size change according the following table:

Table 2.

DIVIDER	LSB	VIRTUAL ACCURACY
---------	-----	------------------

V <sub>REF</sub> (V)	RATIO	(mV)	TO 4.096V FS
4.096	1	4	10-bit
2.048	2	2	11-bit
1.024	4	1	12-bit
0.512	8	0.5	13-bit

The effective resolution remains at 10 bits. But compared to a 4.096V FSR system, the virtual accuracy is improved. The size of 1 LSB remains greater than the typical converter noise floor (300µV), also with divider ratio of 8. This ensures that the ADC performances are not limited by the LSB's reduced size.

µMAX is a registered trademark of Maxim Integrated Products, Inc.

#### Related Parts

<a href="#">MAX159</a>	+2.7V, Low-Power, 2-Channel, 108ksps, Serial 10-Bit ADCs in 8-Pin µMAX	<a href="#">Free Samples</a>
<a href="#">MAX5420</a>	Digitally Programmable Precision Voltage Divider for PGAs	<a href="#">Free Samples</a>
<a href="#">MAX6141</a>	SOT23, Low-Cost, Low-Dropout, 3-Terminal Voltage References	<a href="#">Free Samples</a>

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 2013: <http://www.maximintegrated.com/an2013>

APPLICATION NOTE 2013, AN2013, AN 2013, APP2013, Appnote2013, Appnote 2013

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>