

Option 3 Mod Design Calculations

$$V_P := 0.2 \quad \text{Voltage at OpAmp Non Inverting Input}$$

$$I_{\text{MODMAX}} := 60 \cdot 10^{-3} \quad \text{Maximum Modulation Current}$$

$$I_{\text{MODMIN}} := 20 \cdot 10^{-3} \quad \text{Minimum Modulation Current}$$

$$R_{\text{VARMAX}} := 1000 \quad \text{DS1859 Resistance for Maximum Modulation Current}$$

$$R_{\text{VARMIN}} := 50000 \quad \text{DS1859 Resistance for Maximum Modulation Current}$$

Calculate MODSET Currents

$$I_{\text{MSMAX}} := \frac{I_{\text{MODMAX}}}{270} \quad I_{\text{MSMAX}} = 2.222 \cdot 10^{-4}$$

$$I_{\text{MSMIN}} := \frac{I_{\text{MODMIN}}}{270} \quad I_{\text{MSMIN}} = 7.407 \cdot 10^{-5}$$

Calculate R1 and R2 Divider Values

$$R_1 := 49.9 \cdot 10^3 \quad \text{Pick R1 Value}$$

$$V_{\text{BG}} := 1.2 \quad \text{Bandgap Voltage}$$

$$R_2 := \left(\frac{V_P \cdot R_1}{V_{\text{BG}} - V_P} \right) \quad R_2 = 9.98 \cdot 10^3$$

$$I_{\text{DIV}} := \frac{V_{\text{BG}}}{(R_1 + R_2)} \quad I_{\text{DIV}} = 2.004 \cdot 10^{-5}$$

Calculate R3 and R4 Values

$$R_3 := V_P \cdot \frac{(-I_{MSMIN} \cdot R_{VARMAX} + R_{VARMIN} \cdot I_{MSMAX} - R_{VARMIN} \cdot I_{DIV} + I_{DIV} \cdot R_{VARMAX})}{(-I_{MSMIN} \cdot V_{BG} + I_{MSMIN} \cdot V_P + V_{BG} \cdot I_{MSMAX} - V_P \cdot I_{MSMAX})}$$

$$R_3 = 1.357 \cdot 10^4$$

$$R_4 := \frac{(V_{BG} - V_P) \cdot (R_{VARMIN} - R_{VARMAX})}{-I_{MSMIN} \cdot R_{VARMAX} + R_{VARMIN} \cdot I_{MSMAX} - R_{VARMIN} \cdot I_{DIV} + I_{DIV} \cdot R_{VARMAX}}$$

$$R_4 = 4.873 \cdot 10^3$$

Option 3 APC Design Calculations

$$V_P := 0.2 \quad \text{Voltage at OpAmp Non Inverting Input}$$

$$I_{APC\text{MAX}} := 706 \cdot 10^{-6} \quad \text{Maximum APC Photodiode Current}$$

$$I_{APC\text{MIN}} := 285 \cdot 10^{-6} \quad \text{Minimum APC Photodiode Current}$$

$$R_{V\text{ARMAX}} := 1000 \quad \text{DS1859 Resistance for Maximum APC Current}$$

$$R_{V\text{ARMIN}} := 50000 \quad \text{DS1859 Resistance for Maximum APC Current}$$

Calculate APCSET Currents

$$I_{AS\text{MAX}} := \frac{I_{APC\text{MAX}}}{0.5} \quad I_{AS\text{MAX}} = 0.001$$

$$I_{AS\text{MIN}} := \frac{I_{APC\text{MIN}}}{0.5} \quad I_{AS\text{MIN}} = 5.7 \cdot 10^{-4}$$

Calculate R5 and R6 Divider Values

$$R_5 := 49.9 \cdot 10^3 \quad \text{Pick R5 Value}$$

$$V_{BG} := 1.2 \quad \text{Bandgap Voltage}$$

$$R_6 := \left(\frac{V_P \cdot R_5}{V_{BG} - V_P} \right) \quad R_6 = 9.98 \cdot 10^3$$

$$I_{DIV} := \frac{V_{BG}}{(R_5 + R_6)} \quad I_{DIV} = 2.004 \cdot 10^{-5}$$

Calculate R7 and R8 Values

$$R_7 := V_P \cdot \frac{(-I_{ASMIN} \cdot R_{VARMAX} + R_{VARMIN} \cdot I_{ASMAX} - R_{VARMIN} \cdot I_{DIV} + I_{DIV} \cdot R_{VARMAX})}{(-I_{ASMIN} \cdot V_{BG} + I_{ASMIN} \cdot V_P + V_{BG} \cdot I_{ASMAX} - V_P \cdot I_{ASMAX})}$$

$$R_7 = 1.64 \cdot 10^4$$

$$R_8 := \frac{(V_{BG} - V_P) \cdot (R_{VARMIN} - R_{VARMAX})}{-I_{ASMIN} \cdot R_{VARMAX} + R_{VARMIN} \cdot I_{ASMAX} - R_{VARMIN} \cdot I_{DIV} + I_{DIV} \cdot R_{VARMAX}}$$

$$R_8 = 709.651$$