

Keywords: Sub-1V voltage reference, low dropout, low impedance

#### APPLICATION NOTE 5710

# AN ACCURATE, LOW-IMPEDANCE, LOW-DROPOUT, SUB-1V BANDGAP REFERENCE IS COMPACT AND PROLONGS BATTERY LIFE

*Abstract: A compact, accurate, sub-1V, low-impedance, low-dropout bandgap reference is presented in this paper. The circuit concept presented here is a sub-1V (0.9V in the design example) bandgap reference that can be set from a bit above  $V_{BE}$ , depending on the operating temperature range, and up to the normal bandgap voltage. The circuit idea is realized in 90nm BiCMOS technology. Simulation results show that over a 200°C temperature range, the proposed circuit can achieve 15ppm over line and load regulation. The core can be realized in a CMOS process using parasitic pnp devices.*

A similar version of this article appeared March 10, 2014 in [ELETimes](#).

## Introduction

A voltage reference is a critical building block in most analog circuits. In battery-operated, portable applications the minimum system voltage is continuously being lowered to prolong battery life. The theoretical minimum supply needed for analog circuitry is a threshold plus the saturation voltage of a current source, usually  $V_{DSSAT}$ . For BiCMOS processes, or CMOS processes with parasitic pnp transistors, the minimum operating voltage will be  $V_{BE} + V_{DSSAT}$ , assuming that the CMOS  $V_T$  threshold is lower than  $V_{BE}$ .

In this article a new bandgap reference core is presented that can be set anywhere between slightly above  $V_{BE}$  to  $V_{BG}$ . The lowest output voltage ( $V_O$ ) depends on the lowest temperature that needs to be covered. The design examples below will show that these configurations approach the theoretical minimum operating voltage by 50mV to 100mV from -50°C to +150°C.

Sub-1V voltage references have been realized in different ways before. Engineers have documented<sup>1-5</sup> various architectures in current mode, where CTAT and PTAT currents are generated and added together to a resistor to generate a reference voltage. However, it was shown<sup>6</sup> that those configurations have high noise due to the current mirrors. Because of the mirror mismatches, it is difficult to get the same accuracy using current mirrors compared to the normal bandgap configuration. Without trimming, a well-designed bandgap circuit can normally achieve 3% to 5%<sup>6</sup> accuracy from -40°C to +125°C. Even with a reasonably high overdrive, it is difficult for the current mirrors to achieve this level of accuracy. If overdrive is increased for better matching, it also increases the necessary headroom as  $V_{DSSAT}$  is increased.

There is another way<sup>6,7</sup> to generate a sub-1V reference. The reference voltage is expressed in Equation 1:

$$V_{REF} = kV_{BE} + \Delta V_{BE} = kV_{BE} + V_T \ln(N) \quad (\text{Eq. 1})$$

where N is the ratio of the area of the two emitters.

As shown in Equation 1, the voltage is set in the 100mV to 200mV range. A presentation in 2006<sup>7</sup> gave the design example as  $N = 10$ ,  $V_{REF} = 130\text{mV}$ .

A reference voltage close to ground is not desirable because the noise and the offset in the next stage will be proportionally larger than the reference voltage. Consequently, the overall accuracy deteriorates. This article presents a novel approach that resolves the aforementioned issues and provides superior performance. For example, a 0.9V reference can be generated with a 1.0V supply or lower, depending on the load.

### The New Proposed Core for a Sub-1V Reference

#### A BiCMOS Process with npns

Figure 1 shows the proposed core.

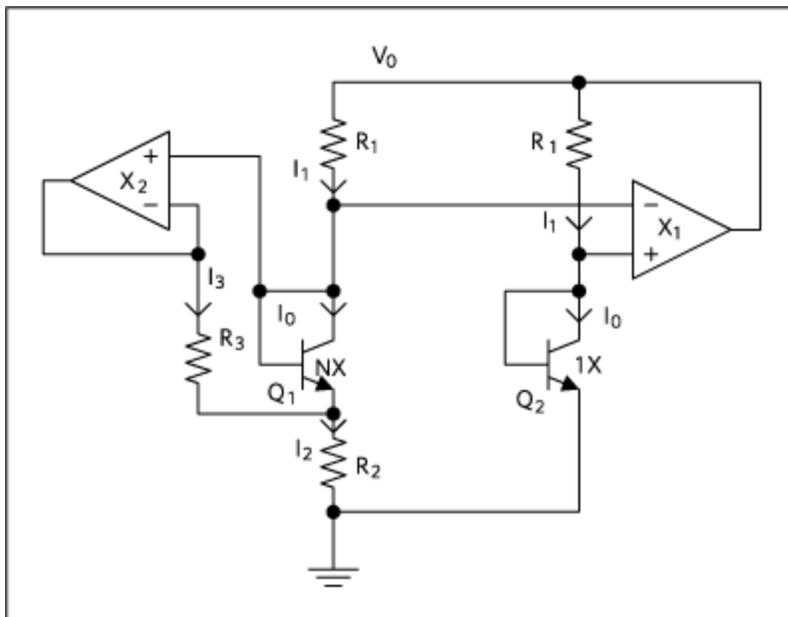


Figure 1. New bandgap core.



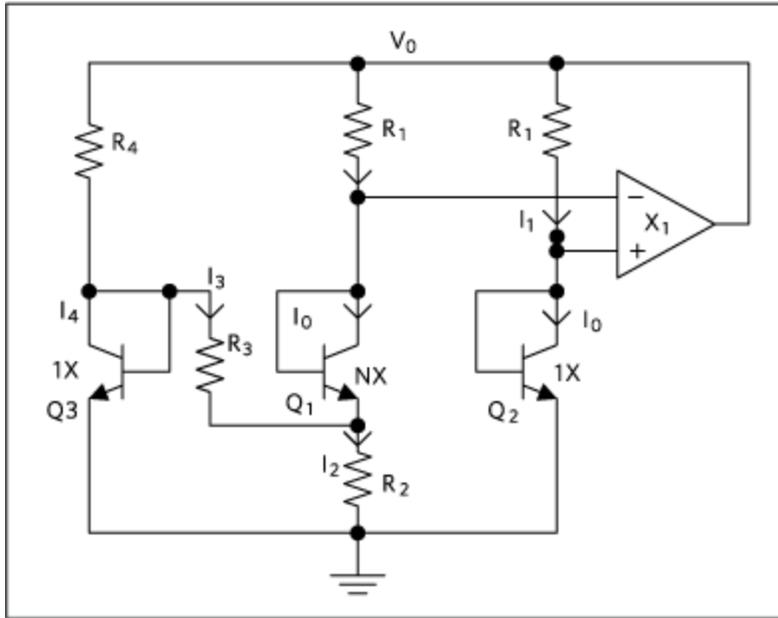


Figure 3. Simplified version of the proposed npn core.

As a design example for this core,  $V_0 = 0.9V$  is chosen.

For low-power applications, the quiescent current ( $I_Q$ ) is targeted in the  $\mu A$  range. Based on the configuration in Figure 3, we have three variables,  $R_1$ ,  $R_2$ , and  $R_3$ , and two equations, (Equation 3 and Equation 4), defined by  $V_0$  and  $V_{BG}$ . Therefore,  $I_2$  is chosen to get one more equation to derive all three resistor values.

From Equation 3:

$$R_2 = (V_T \times \ln N) / I_2 \quad (\text{Eq. 5})$$

From Equations 4 and 5:

$$R_1 = \frac{V_{BG} \times \left(1 - \frac{V_T \times \ln N}{V_0}\right) - V_{BE1}}{I_2 \times \frac{V_{BG}}{V_0}} \quad (\text{Eq. 6})$$

$$R_3 = \frac{R_1}{1 - \frac{V_0}{V_{BG}}} \quad (\text{Eq. 7})$$

There is no individual knob to control the output voltage and its TC separately. Here is the procedure to fine-

tune the circuit to the zero TC point and to obtain the desired output voltage.

1. Find the exact  $V_{BE1}$  voltage in simulation.
2. Find  $V_{BG}$  by adjusting  $R_2$  until  $V_0$  is zero TC. Now follow this procedure: increase  $R_2$  if  $V_0$  has a positive TC; decrease  $R_2$  if  $V_0$  has a negative TC. Note the value of zero TC  $V_0$ , then:

$$V_{BG} = V_0 / (1 - R_1/R_3) \quad (\text{Eq. 8})$$

3. Recalculate  $R_1$ ,  $R_2$ , and  $R_3$  using the new  $V_{BG}$  and  $V_{BE}$  values.

$$V_{BG} = 1.203V$$

$$V_{BE1} = 0.58V$$

$$I_2 = 1.0\mu A$$

$$N = 8$$

$$R_4 = \frac{1}{2}R_1 = 206k \quad .$$

The final calculated design parameters are shown in **Table 1**:

**Table 1. Calculated Values for Design Example**

$^{\circ}C$	<b>-55</b>	<b>25</b>	<b>150</b>
$V_{BE1}$	0.74	<b>0.58</b>	0.33
$V_{BG}$	1.203	1.203	1.203
$V_T$	0.019	<b>0.026</b>	0.036906
$I_2$	7.32E-07	<b>1.00E-06</b>	1.42E-06
$I_3$	4.52E-07	3.55E-07	2.02E-07
$I_0$	2.79E-07	6.45E-07	1.22E-06
$I_1$	2.79E-07	6.45E-07	1.22E-06
$R_1$	4.120E+05	4.120E+05	4.120E+05
$R_2$	5.407E+04	5.407E+04	5.407E+04
$R_3$	1.636E+06	1.636E+06	1.636E+06
$R_4$	2.060E+05	2.060E+05	2.060E+05

Realizing Figure 3 in a 90nm BiCMOS process with transistor circuitry, the simulation results are plotted in **Figure 4**. The typical case is: supply voltage = 1.5V; output load = 10 $\mu$ A; all process corners (bipolar, CMOS, resistor, capacitor) having line and load combinations with supply voltage = ( $V_0 + 0.1V$ ) and 1.65V; output load = 0 $\mu$ A and 20 $\mu$ A. The circuit has temperature compensation and 0.1% LSB trim. The results show that  $V_0$  stays within 2.6mV, less than  $\pm 0.15\%$  from  $-50^{\circ}C$  to  $+150^{\circ}C$ , or 15ppm over line and load. With processes variation and 0.1% LSB trimming, this bandgap voltage reference can achieve  $\pm 0.45\%$  accuracy over 200 $^{\circ}C$  temperature range.

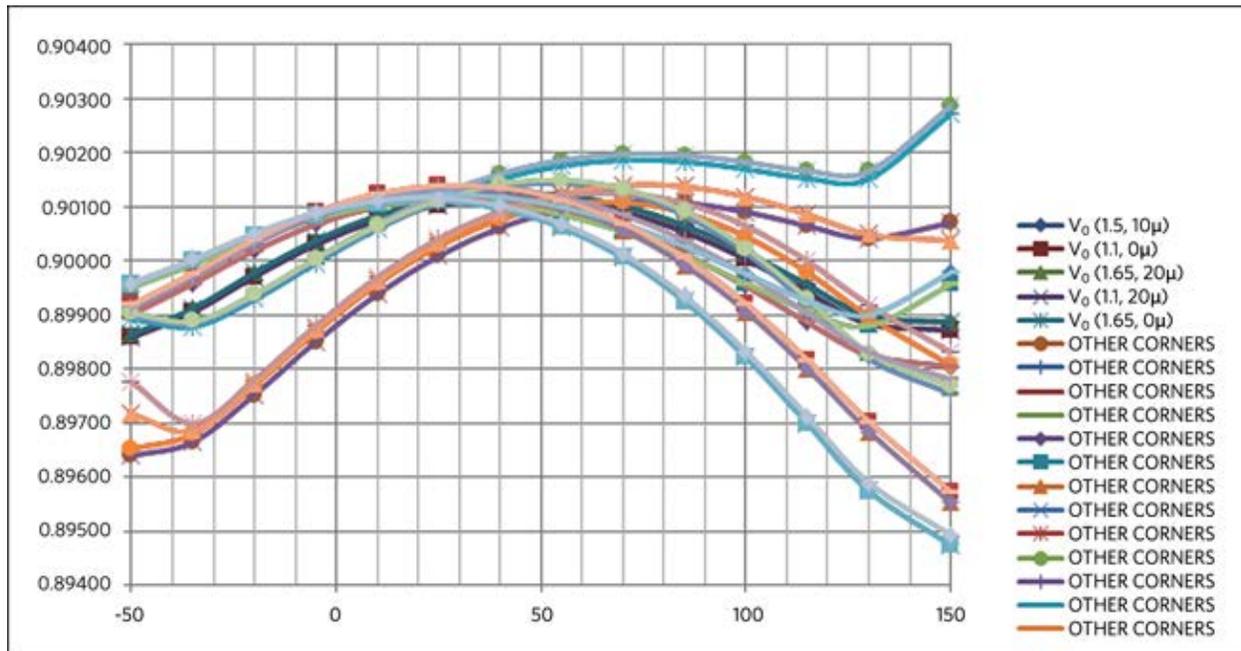


Figure 4. Simulation results of npn core.

## Performance Comparison

Table 2 compares the performance of proposed cores with existing designs:

Table 2. Performance Comparison Table for Different Sub-1V Bandgap Circuits

	Proposed Core	Reference 5	Reference 3	Reference 6
Tech/m	90n BiCMOS	500n CMOS	600n CMOS	500n BiCMOS
$V_{DD}/V$	1-1.65*	0.93-5	0.98-1.5	1 up
$V_{REF}/mV$	900	228	603	190.9
TC/ppm	15	34	34.7	11
$I_Q/\mu A$	6	28	18	20
PSRR/dB	-84	-58	-	-
@100Hz	-62.2	-	-44	-
@10kHz	-28.6	-12	-	-
@1MHz				
Noise/(nV/ Hz) @100Hz	1573	200	-	40
Area/mm <sup>2</sup>	0.023**	0.0464	0.24	0.4

\*It uses 1.65V devices, so the maximum voltage is 1.65V. If a 4.5V device is used, it can go up to 4.5V.

\*\*Die size is based on placement of all components in corresponding wells with DRC cleaned.

## Conclusion

This article shows an elegant way of creating a compact, sub-1V bandgap reference in a low-dropout and low-impedance configuration. This proposed solution has a superior accuracy of about 20ppm with load, line regulation, and temperature variation. The headroom requirement approaches the theoretical minimum. The die size is comparable with a traditional bandgap reference with three more components (2 resistors and 1 npn). This design is small and can enhance the circuitry working with a lower battery voltage that is beneficial, even critical to portable designs.

## References

1. H. Banba et al, "A CMOS bandgap reference circuit with sub-1-V operation," **IEEE J. Solid State Circuits**, vol. 34, no. 5, pp. 670-674, May 1999.
2. P. Malcovati et al., "Curvature compensated BiCMOS bandgap with 1-V supply voltage," **IEEE J. Solid-State Circuits**, vol. 36, no. 7, pp. 1076-1081, Jul 2001.
3. K.N. Leung and Philip K. T. Mok, "A sub-1-V 15ppm/C CMOS bandgap voltage reference without requiring low threshold voltage device," **IEEE J. Solid-State Circuits**, vol. 37, no. 4 pp. 526-530, Apr, 2002.
4. Zhidong Liu and Yuhua Cheng, "A Sub-1V CMOS Bandgap Reference with High-order Curvature Compensation," **IEEE International Conference of Electron Devices and Solid-State Circuits**, 2009 EDSSC.
5. David C. W. Ng, David K. K. Kwong, and Ngai Wong, "A sub-1V, 26uW, low-output-impedance CMOS Bandgap Reference with a low Dropout or Source Follower Mode," **IEEE Transactions on VLSI Systems**, Vol. 19, No. 7 July 2011.
6. Keith Sanborn, Dongsheng Ma, and Vadim Ivanov, "A sub-1-V Low-Noise Bandgap Voltage Reference," **IEEE Journal of Solid-State Circuits**, vol. 42, no. 11, November 2007.
7. I.M. Filanovsky, V. Ivanov, K.E. Sanborn, University of Alberta, Edmonton, Canada, Texas Instruments, "Sub-1V Supply Bandgap voltage references based on Asymmetric Differential Pair," **49th IEEE International Midwest Symposium on Circuits and Systems (MWSCAS)**, Vol. 2, 2006.

## General References

G. Giustolisi, G. Palumbo, M. Criscione, and F. Cutri, "A low-voltage low-power voltage reference based on subthreshold MOSFETs," **IEEE Journal of Solid-State Circuits**, Vol. 38, No. 1, pp. 151-154 January 2003.

Giuseppe De Vita and Giuseppe Iannaccone, "A sub1V, 10ppm/C, Nanopower Voltage Reference Generator," **IEEE Journal of Solid-State Circuits**, Vol. 42. No 7, pp. 1536-1542, July 2007.

Related Parts		
<a href="#">MAX6023</a>	Precision, Low-Power, Low-Dropout, UCSP Voltage Reference	<a href="#">Free Samples</a>
<a href="#">MAX6034</a>	Precision, Micropower, Low-Dropout, SC70 Series Voltage Reference	<a href="#">Free Samples</a>
<a href="#">MAX6035</a>	High-Supply-Voltage, Precision Voltage Reference in SOT23	<a href="#">Free Samples</a>
<a href="#">MAX6100</a>	Low-Cost, Micropower, Low-Dropout, High-Output-Current, SOT23 Voltage References	<a href="#">Free Samples</a>
<a href="#">MAX6101</a>	Low-Cost, Micropower, Low-Dropout, High-Output-Current, SOT23 Voltage References	<a href="#">Free Samples</a>
<a href="#">MAX6102</a>	Low-Cost, Micropower, Low-Dropout, High-Output-Current, SOT23 Voltage References	<a href="#">Free Samples</a>
<a href="#">MAX6103</a>	Low-Cost, Micropower, Low-Dropout, High-Output-Current, SOT23 Voltage References	<a href="#">Free Samples</a>
<a href="#">MAX6104</a>	Low-Cost, Micropower, Low-Dropout, High-Output-Current, SOT23 Voltage References	<a href="#">Free Samples</a>
<a href="#">MAX6105</a>	Low-Cost, Micropower, Low-Dropout, High-Output-Current, SOT23 Voltage References	<a href="#">Free Samples</a>
<a href="#">MAX6106</a>	Low-Cost, Micropower, Low-Dropout, High-Output-Current, SOT23 Voltage References	<a href="#">Free Samples</a>
<a href="#">MAX6107</a>	Low-Cost, Micropower, Low-Dropout, High-Output-Current, SOT23 Voltage References	<a href="#">Free Samples</a>

---

### More Information

For Technical Support: <http://www.maximintegrated.com/en/support>

For Samples: <http://www.maximintegrated.com/en/samples>

Other Questions and Comments: <http://www.maximintegrated.com/en/contact>

---

Application Note 5710: <http://www.maximintegrated.com/en/an5710>

APPLICATION NOTE 5710, AN5710, AN 5710, APP5710, Appnote5710, Appnote 5710

© 2014 Maxim Integrated Products, Inc.

The content on this webpage is protected by copyright laws of the United States and of foreign countries.

For requests to copy this content, [contact us](#).

Additional Legal Notices: <http://www.maximintegrated.com/en/legal>