

# Quad Output Power Reference Design with Input Fault Protection for Automotive Applications

Terry Lo, Automotive Power Systems Engineering Manager  
 Fil Paulo Balat, Applications Development Manager  
 Siglo Raphael Alcantara, Applications Development Engineer, and  
 Michael Lacson, Senior Applications Development Engineer

## Abstract

A quad output, triple monolithic buck converter and boost controller reference design is presented that applies to automotive electronics such as a telematics box. The reference design features a fault protection scheme to support against input transients such as load dump, cold crank, or reverse battery.

## Introduction

Voltage transients from the energy generated by the car alternator and ignition system, or fault events due to external factors such as a car crash, can affect the electronic circuitry in an automotive system. Reliability of the electronic circuitry may be greatly affected; therefore, protection against these unpredictable events must be considered. A telematics box, for example, is an electronic system inside the car that requires high reliability and protection.

The power system design in this article is a reference design solution to provide protection and reliability to a car electronic module that requires four voltage inputs. It features input fault protection against load dump, cold crank, and reverse battery. A PowerPath™ controller allows smooth switch-over between the main and backup batteries when input fault protection is active. A quad output regulator provides four voltage outputs with a triple monolithic buck converter and a boost controller. One of the buck outputs can be made to handle high output peak current requirements, such as those on a communication module. There is a provision for charging the backup battery through a linear battery charger when the main battery is active. Figures 1 and 2 show the basic block diagram and the evaluation board of the reference design solution.

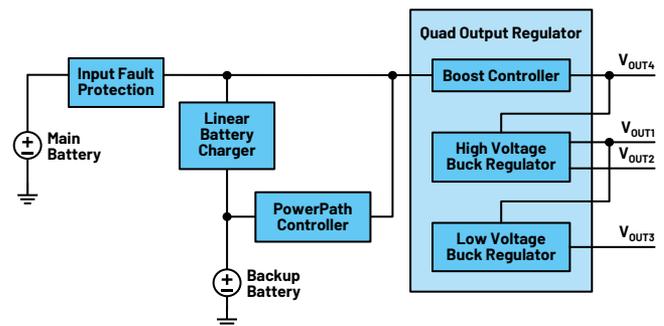


Figure 1. Basic block diagram of the reference design.

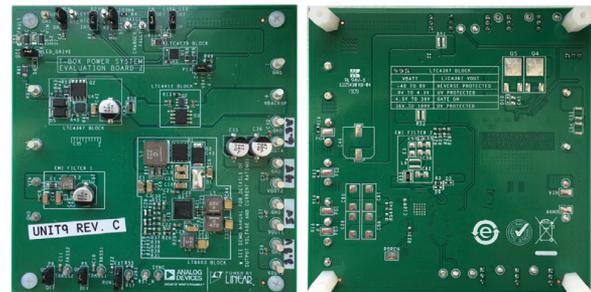


Figure 2. Evaluation board hardware.

## Fault Events and Scenarios

### Load Dump

Load dump occurs when the alternator system is charging a battery and the connection to the battery is lost. A battery may be disconnected because of cable degradation, improper connection, or purposeful separation while the engine is running, resulting in a load dump. Alternator systems without centralized load dump suppression allow the alternator to produce extremely high voltages in the event of a sudden battery disconnection. The voltage dumped onto the load can go up to 100 V for a 12 V system due to the stator's high inductance and the vehicle's voltage regulator's inability to reduce the field current rapidly enough.

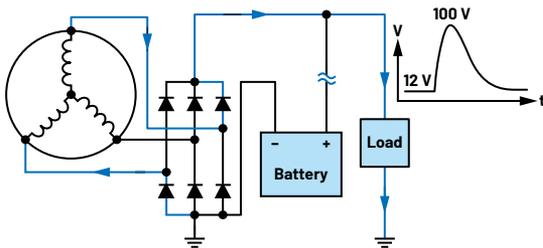


Figure 3. A load dump scenario.

### Cold Crank

During startup or cranking, the engine requires more power, causing the battery voltage to dip. In general, starting an engine in a cold environment is harder than starting an engine in a warm environment. This requires the engine to draw more power, which results in a larger voltage drop compared to normal cranking. This condition is known as cold crank. The waveform in Figure 4 shows the waveform during cold crank where the main battery falls below its specified level.

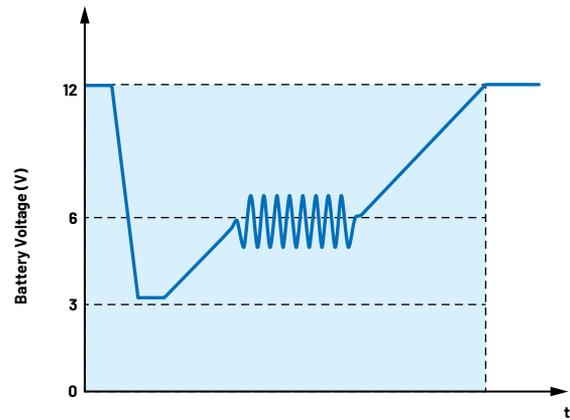


Figure 4. A sample cold crank scenario.

### Reverse Voltage

A reverse voltage or, simply, reverse battery condition covers the human error scenario where someone connects a battery with the polarity reversed. This can result in destruction unless adequate protection is provided.

### Circuit Function

#### Fault Protection

The LTC4367 serves as a fault protection for the circuit as it disconnects the  $V_{BATT}$  voltage to  $V_{IN}$  when the  $V_{BATT}$  voltage is too low, too high, or negative. It has accurate overvoltage and undervoltage comparators to ensure that power is applied to the system only if the input supply is within the allowable voltage window. The LTC4367 automatically isolates the load from negative input voltages. It can operate an overvoltage protection that can go as high as 100 V and undervoltage protection that can go as low as -40 V.

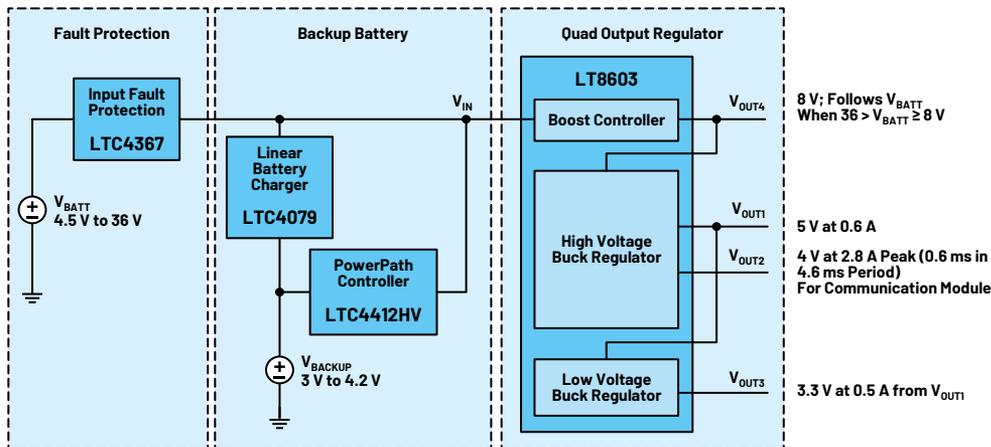


Figure 5. Block diagram of a typical circuit and its function.

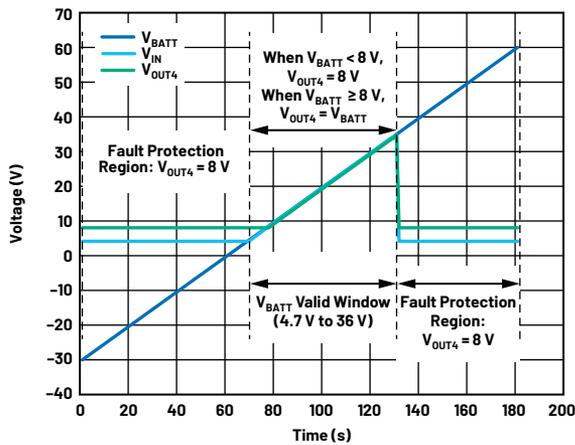


Figure 6.  $V_{BATT}$  valid and fault protection window.

### Backup Battery

Backup battery charging is possible through the [LTC4079](#), which features a multi-chemistry battery charger that allows a flexible battery voltage to be used. With the reference design circuit, a charging voltage of around 4.2 V is used. To avoid overcharging the battery, the LTC4079 also features a charge termination capability through a C/10 detector or a set charge timer of around 2 hours and 30 minutes.

Automatic switch-over between  $V_{BATT}$  and  $V_{BACKUP}$  is possible through the [LTC4412](#) PowerPath controller. This feature allows the [LT8603](#) to maintain an output voltage on  $V_{OUT4}$ , by having a  $V_{IN}$  drawing from either  $V_{BATT}$  or  $V_{BACKUP}$ . In the event

of  $V_{BATT}$  disconnection or fault detected, the controller allows the current to flow from the  $V_{BACKUP}$  to the  $V_{IN}$  of the LT8603. When no fault is detected, the LTC4412 will block the path connecting the  $V_{BACKUP}$  to the  $V_{IN}$  of the LT8603. Figure 7 shows the waveform of the power switch-over event.

In the event of a cold crank,  $V_{BATT}$  goes down from 12 V to 2 V. The  $V_{BATT}$  path is disconnected, and  $V_{BACKUP}$  now serves as the  $V_{IN}$  of the boost converter in order to maintain an 8 V output on  $V_{OUT4}$ . When  $V_{BATT}$  increases to ~5 V, it will again serve as the  $V_{IN}$  for the boost converter.  $V_{OUT4}$  will still be maintained at 8 V until  $V_{BATT}$  reaches 8 V. As  $V_{BATT}$  recovers to its original voltage of 12 V,  $V_{OUT4}$  will then follow the voltage of  $V_{BATT}$ . A small voltage drop on  $V_{OUT4}$  is due to the diode forward voltage. The power switch-over allows  $V_{OUT1}$ ,  $V_{OUT2}$ , and  $V_{OUT3}$  to maintain its regulation.

### Quad Output Regulator

The LT8603 features a boost regulator,  $V_{OUT4}$ , with two high voltage buck regulators,  $V_{OUT1}$  and  $V_{OUT2}$ , and a low voltage buck regulator,  $V_{OUT3}$ . The boost regulator is capable of providing power to the buck regulators. The LT8603 provides good input and output load regulation at different input voltage levels. Figure 8 shows the output regulation of the LT8603.

The high output peak current capability of one of the buck regulator outputs,  $V_{OUT2}$ , of the LT8603 is used for applications that involve a communication module. A typical 3.6 V to 4 V output voltage and an output peak current on-time of 0.6 ms over a 4.6 ms period is required for a communication module. On the tested conditions shown in Figure 9, the system's transient behavior is monitored.  $V_{OUT2}$  features a good transient response with minimal voltage undershoot and overshoot.

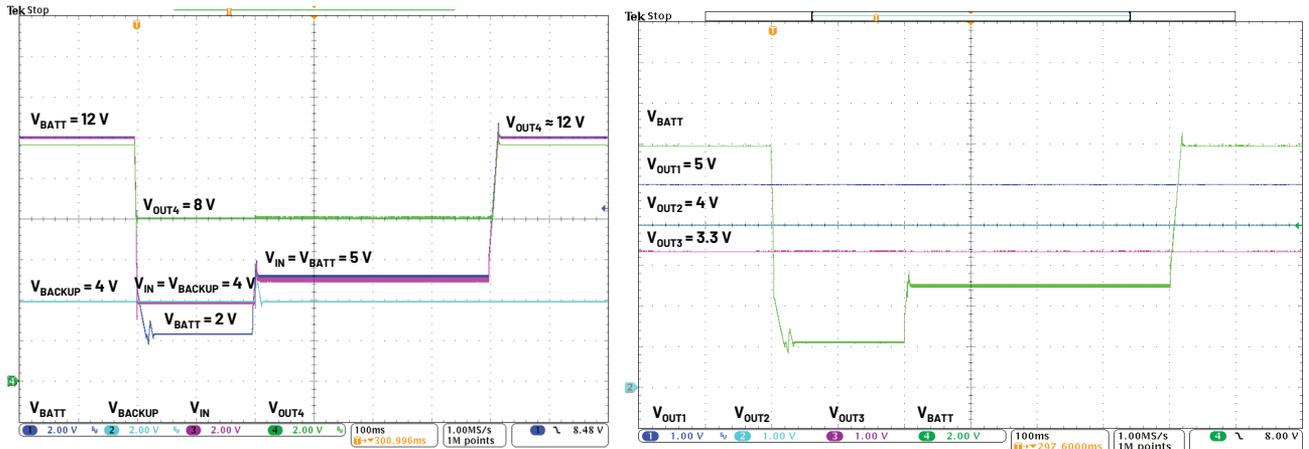


Figure 7. Power switch-over event at cold crank.

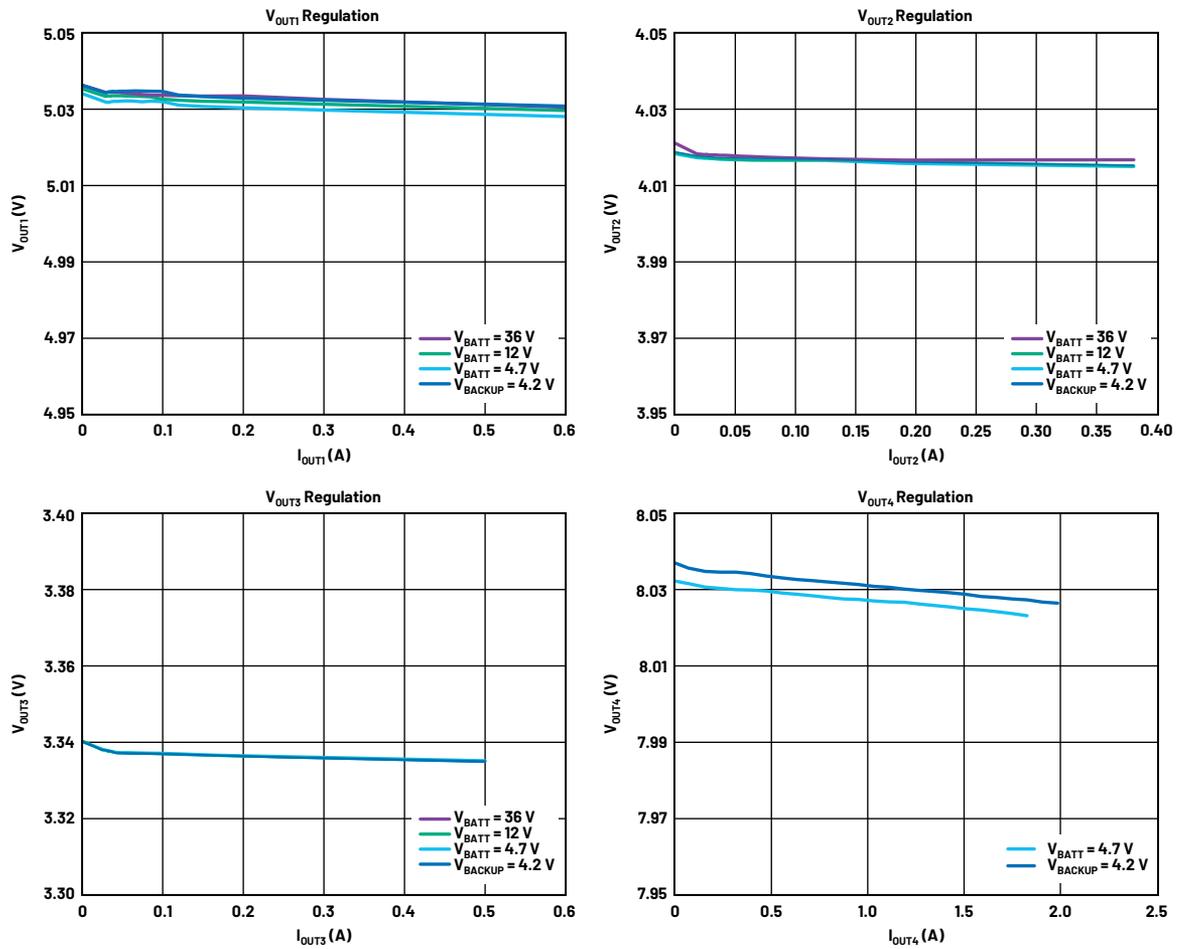


Figure 8. Output regulation of the LT8603.

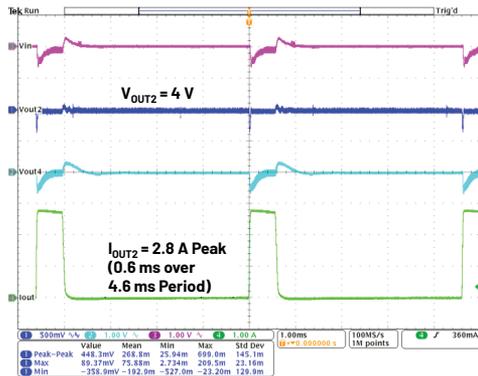


Figure 9. High output peak current performance of V<sub>OUT2</sub>.

### Load Dump Response

The input fault protection and power switch-over feature of the reference design board allows the LT8603 to operate despite being in a load dump event. Figure 10 shows a simulated waveform of a load dump condition where V<sub>BATT</sub> goes as high as 100 V and the response of the boost, V<sub>OUT4</sub>, and one of the buck regulators, V<sub>OUT3</sub>. During the overshoot due to load dumping, the 36 V V<sub>BATT</sub> limit is reached and the LTC4367 disconnects the path connecting V<sub>BATT</sub> to V<sub>IN</sub>. V<sub>OUT4</sub> now sources its V<sub>IN</sub> from V<sub>BACKUP</sub> to maintain the regulated 8 V level. As V<sub>BATT</sub> restores to its original level, V<sub>OUT4</sub> will then follow V<sub>BATT</sub>.

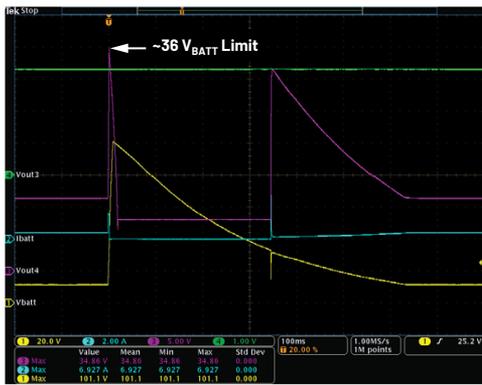


Figure 10. Load dump response.

## Circuit Variations and Implementations

The flexibility of the schematic design allows variations on how the circuitry can be implemented. The reference design board has “Do Not Install” components and path connectors that allow the user to configure the board with either Topology 1 or Topology 2. This also allows the configuration of either a boost or SEPIC converter on  $V_{OUT4}$  depending on the application. An additional circuit option for added input fault protection can be implemented on the LTC4367 for 150 V transient conditions. More details on the configuration are shown on the schematic of the reference design board.

The circuit configuration presented in Figure 5 is Topology 1, which has a minimum  $V_{BACKUP}$  voltage of 2.5 V, one EMI filter after  $V_{IN}$ , and is capable of power switch-over through the LTC4412HV. The  $V_{IN}$  of the boost controller sources its

power from  $V_{BATT}$  or  $V_{BACKUP}$ . During the  $V_{BATT}$  valid window,  $V_{OUT4}$  maintains a regulated voltage level through the boost converter or follows  $V_{BATT}$  as shown in Figure 6. Outside the  $V_{BATT}$  valid window,  $V_{OUT4}$  sources from  $V_{BACKUP}$  in order to maintain a regulated set level.

Topology 2 addresses the need for a lower  $V_{BACKUP}$  voltage application such as a 1.5 V level. When there is no input fault,  $V_{BATT}$  is directly connected to  $V_{OUT4}$  while  $V_{BACKUP}$  is the  $V_{IN}$  to the boost controller. Additional filters are required on the input of the buck regulators for better noise filtering and EMI performance. Power switch-over is achieved seamlessly when  $V_{BATT}$  falls below or goes above its valid window. The minimum  $V_{BATT}$  voltage level of the valid window is set to the regulated level of  $V_{OUT4}$ . During the  $V_{BATT}$  valid window,  $V_{OUT4}$  follows  $V_{BATT}$ . Outside of the  $V_{BATT}$  valid window,  $V_{BACKUP}$  is used to maintain a regulated set level.

Table 1. Comparison Between Topology 1 and 2

	Topology 1	Topology 2
ICs Used	LT8603, LTC4412HV, LTC4367, LTC4079	LT8603, LTC4367, LTC4079
Backup Battery Operation	$V_{BACKUP}$ operates as low as 2.5 V	$V_{BACKUP}$ operates as low as 1.5 V
EMI Input Filtering	Connected before boost regulator	Connected before boost and buck regulators input
Minimum $V_{BATT}$ Valid Window	$V_{BATT}$ can go as low as the $V_{BACKUP}$ level	$V_{BATT}$ must be equal to $V_{OUT4}$ regulated set level

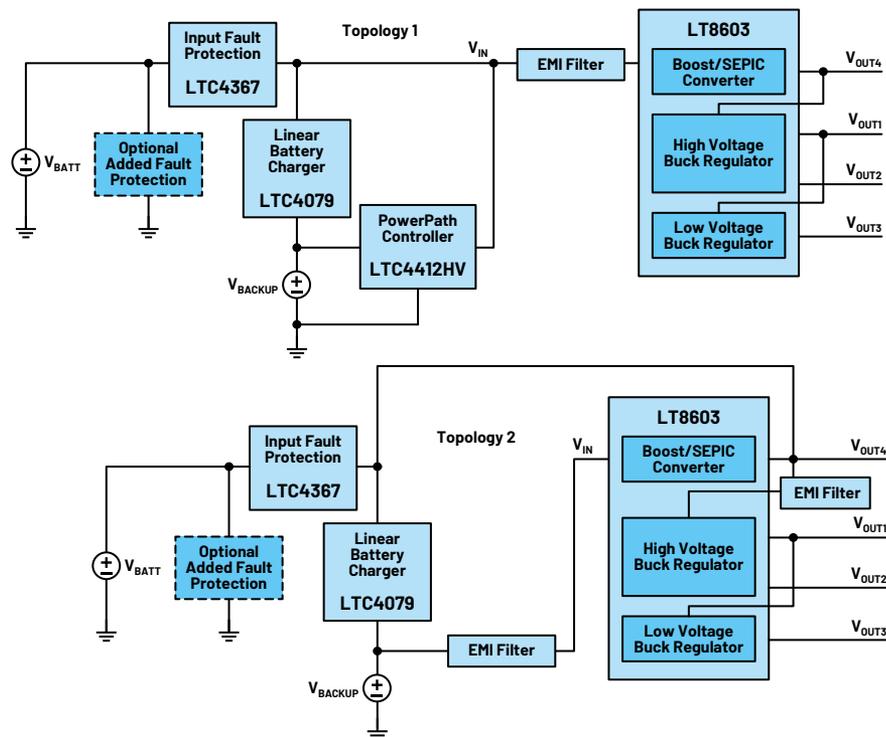


Figure 11. Circuit variations.

## Conclusion

The ever-growing advancement of automotive applications requires more reliability and safety considerations. The standards defined by international organizations have played a significant role for designers focusing on what contributes to the voltage transients that may be harmful or can cause degradation of the electronic system. In conclusion, the quad output power reference design has proven its capability when exposed to the simulated test conditions of input overvoltage, undervoltage, and reverse voltage operations. Also, the different circuit variations allow flexibility with regards to the backup battery operation, minimum battery voltage level, EMI input filtering, and the number of components. For more information about the reference design board, contact the authors or your local ADI representative.

## Reference Design ICs and Files

Attached [here](#) are the schematic, PCB Gerber files, and the bill of materials (Topology 1) of the quad output regulator. For evaluation board availability, contact the authors or your local ADI representative.

## References

Eddleman, Dan. "Low Quiescent Current Surge Stopper: Robust Automotive Supply Protection for ISO 7637-2 and ISO 16750-2 Compliance." Analog Devices, Inc., January 2017.

Eddleman, Dan. "LTspice: Models of ISO 7637-2 & ISO 16750-2 Transients." Analog Devices, Inc.

ISO 16750-2:2012: Road Vehicles—Environmental Conditions and Testing for Electrical and Electronic Equipment—Part 2: Electrical Loads. International Organization for Standardization, November 2012.

Wu, Bin and Zhongming Ye. "Comprehensive Power Supply System Designs for Harsh Automotive Environments Consume Minimal Space, Preserve Battery Charge, Feature Low EMI." *Analog Dialogue*, Vol. 53, No. 3, August 2019.

## About the Authors

Terry Lo received his B.Eng. (Hon.) degree from The University of Hong Kong in 1992 and his M.Sc. degree in electronic engineering from City University of Hong Kong in 1998. In 1999, Terry joined Linear Technology (now part of Analog Devices) as a field applications engineer, and he moved to the U.S. in 2016. He is now a power system engineering manager. Terry enjoys painting in his leisure. He can be reached at [terry.lo@analog.com](mailto:terry.lo@analog.com).

Fil Balat is an applications development manager in the Power Business Unit. He joined Analog Devices in 2016. He has more than 20 years of power supply design experience working at companies such as Emerson Network Power, Flextronics, and now Analog Devices. Fil's product focus is on power management for automotive applications and general-purpose DC-to-DC converters in different topologies such as flyback, buck, boost, 4-switch, inverting buck-boost, and SEPIC. He can be reached at [fil.balat@analog.com](mailto:fil.balat@analog.com).

Siglo Raphael Alcantara joined Analog Devices in October 2020 as a product applications engineer under the power team. His work focuses on the development of power management for automotive applications. He graduated from the University of Santo Tomas in Manila City, Philippines, with a bachelor's degree in electronics engineering. He can be reached at [sigloraphael.alcantara@analog.com](mailto:sigloraphael.alcantara@analog.com).

Michael Angelo Lacson is an applications engineer in the Power Business Unit. He joined Analog Devices in 2018. He has more than eight years of power supply design experience working at Artesyn Embedded Technologies and now Analog Devices. Michael previously worked on power solutions for automotive and FPGA applications. He is now focusing on ADI's line of  $\mu$ Module<sup>®</sup> products. He earned a bachelor's degree in electronics engineering from De La Salle University Manila, Philippines, and a post-graduate diploma in power electronics from Mapúa University, Manila, Philippines. He can be reached at [mikee.lacson@analog.com](mailto:mikee.lacson@analog.com).

Engage with the ADI technology experts in our online support community. Ask your tough design questions, browse FAQs, or join a conversation.



Visit [ez.analog.com](https://ez.analog.com)



AHEAD OF WHAT'S POSSIBLE™

For regional headquarters, sales, and distributors or to contact customer service and technical support, visit [analog.com/contact](https://analog.com/contact).

Ask our ADI technology experts tough questions, browse FAQs, or join a conversation at the EngineerZone Online Support Community. Visit [ez.analog.com](https://ez.analog.com).

©2022 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.

TA23289-1/22

VISIT [ANALOG.COM](https://analog.com)